

Aerospace Consulting LLC

P.O. Box 536, Buckingham, Pa. 18912

215-345-7184 215-345-1309 FAX

RFandMicrowaveDesign.com

Using Simulation Tools to Troubleshoot an LC Filter Design

By Ed Troy

Almost everyone uses simulation tools for designing RF, microwave, and high speed digital circuits today. It is essential. But, very few engineers use those same tools for troubleshooting of circuits that are not working correctly. It amazes me that many engineers and technicians still spend days tuning, tweaking, and adjusting RF circuits that do not work properly on the bench. They could probably find, and fix, the problems in much less time by firing up their simulation software. It is much faster to change values, both known and speculated, in a simulation engine than it is to make the same changes on the test bench.

I was first introduced to the power of using simulation to troubleshoot circuits in the early 1980's. I was working on a receiver that required a 70 MHz IF band pass filter. While many people may consider 70 MHz to be VHF, or very high frequency, or even UHF, or ultra high frequency, I thought of it as a pretty low frequency, since I was used to working at frequencies up to 18 GHz.

But, when my technician tested a 70 MHz band pass filter that I had designed, it did not work at all as expected. In fact, the performance was so bad that I thought that perhaps someone had mixed up the capacitors or inductors and thus installed the wrong values. So, I had the technician rebuild the circuit using components whose values had been actually measured. The results were the same. The filter looked terrible.

This happened over 30 years ago, so I do not have the original design files or test results, but I can reproduce them very easily in a circuit simulator. Lets say we need a 70 MHz band pass filter with a bandwidth of 5 MHz. A few minutes with the Keysight (formerly Agilent) Genesys filter design tool produces the following circuit (figure 1) and response (figure 2).

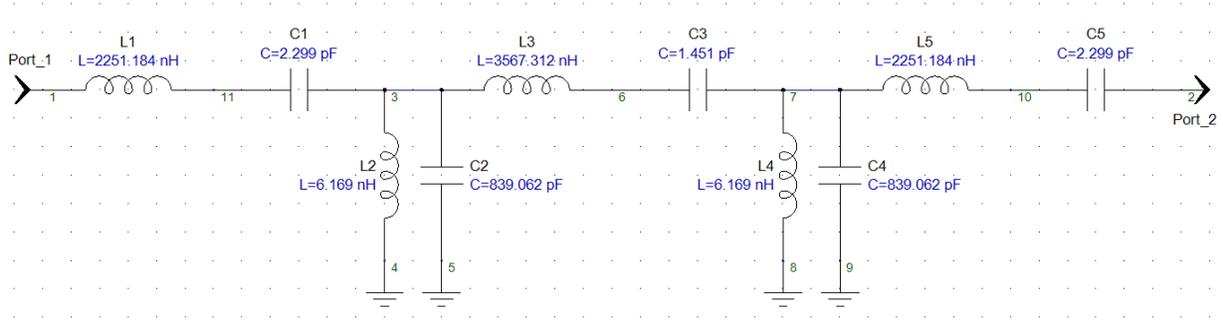


Figure 1 Ideal 70 MHz Band Pass filter design

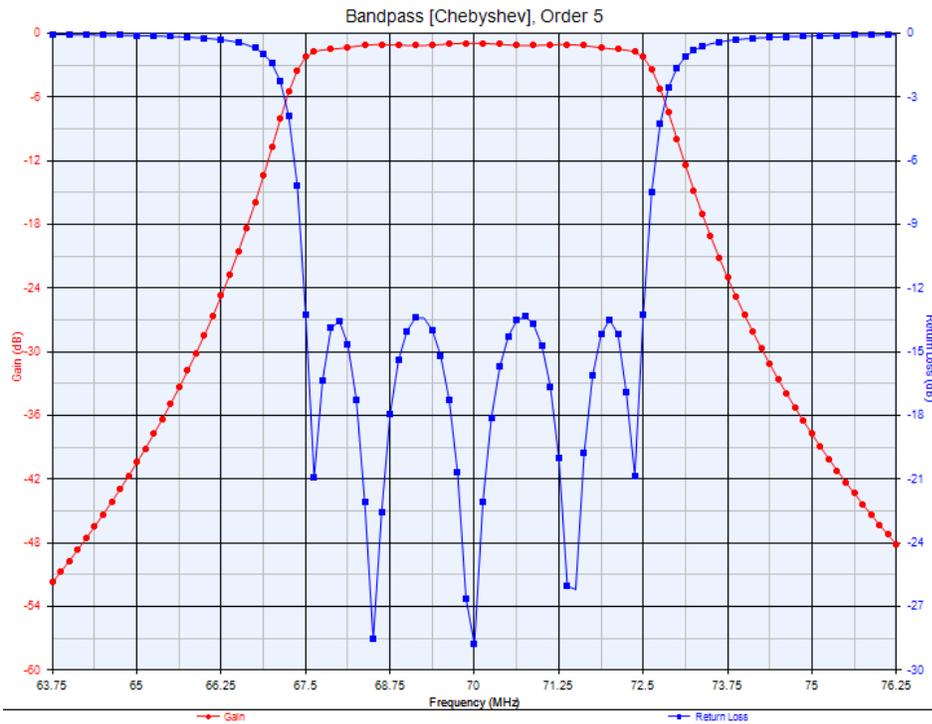


Figure 2 Filter response of filter in figure 1

This looks pretty good! But, when my technician built it up, as I said, we got a response similar to what is shown in figure 3.

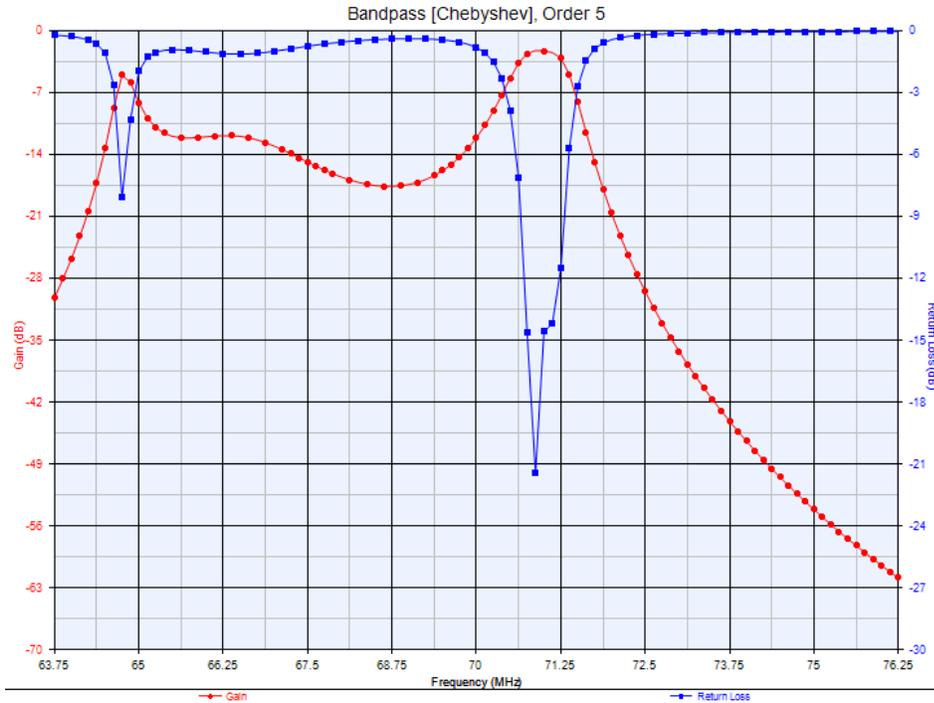


Figure 3 Measured response of circuit in figure 1

OOPS! Something is obviously wrong. But, we measured the values and the inductors and capacitors were the correct values. What could be wrong?

After looking at the situation for a while, I realized that there was a pad on the circuit board where L1 and C1, L3 and C3, and L5 and C5 came together. Those pads were only about .1"x.1" in size, however. How could those tiny pads matter? A quick calculation showed that those pads had a capacitance to ground of about 0.22 pF. How did I come to that conclusion? By using the equation for a parallel plate capacitor. In our case, k, the relative dielectric constant of our circuit board material was 3.3. Eo is a physical constant. The necessary calculations are shown below, where the equation for the capacitance of a parallel plate capacitor is shown by the equation for C0:

$$E_0 := 8.854 \cdot 10^{-12} \frac{\text{F}}{\text{m}}$$

Since the pad is 100 mils square, or .1" x .1", and there are .0254 m/in

$$A_0 := (.1 \cdot .0254)^2 \text{ m}^2$$

$$A_0 = 6.452 \times 10^{-6} \text{ m}^2$$

The board thickness was 33 mils, or .033 inches, or .033*.0254 meters

$$d := .033 \cdot .0254 \text{ m} \quad d = 8.382 \times 10^{-4} \text{ m}$$

$$C_0 := \frac{(k \cdot E_0 \cdot A_0)}{d}$$

$$C_0 = 2.249 \times 10^{-13} \text{ F} \quad \text{which is } .2249 \text{ pF}$$

Again, so what? Well, let's re-simulate the circuit putting .2 pF capacitors at those points, as shown in figure 4.

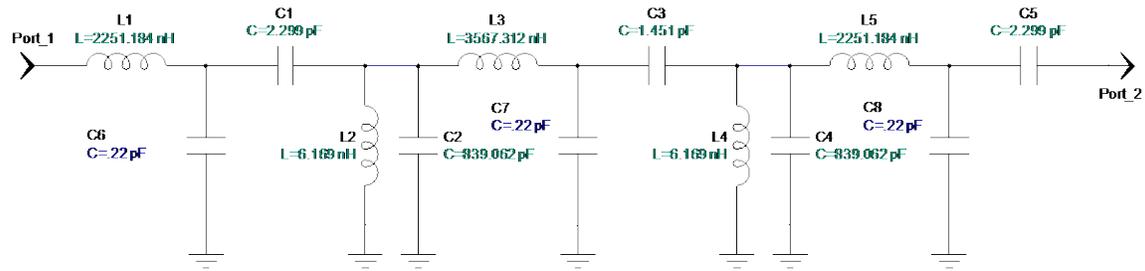


Figure 4 Filter circuit with calculated spurious capacitances added to schematic

The result of that re-simulation is shown in figure 5.

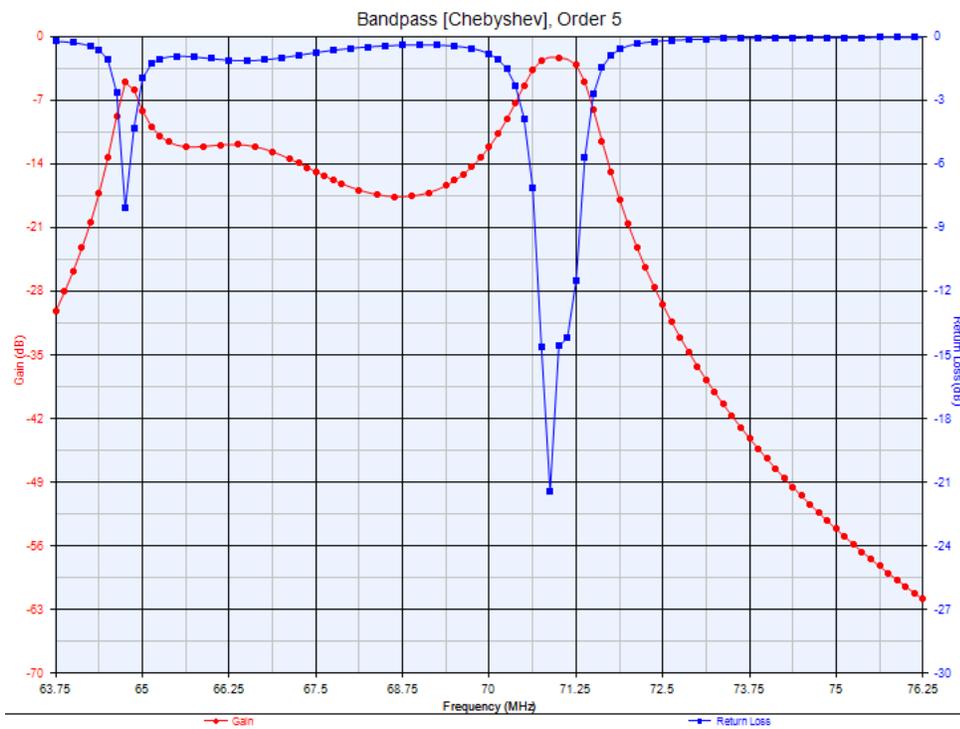


Figure 5 Simulation result for circuit in figure 4

This is the same as the measured result. (Of course it is the same in this case since I used the simulator with the .2 pF capacitors added to produce the "measured" result. But, trust me, the result we saw when we measured the filter circuit in the early 1980's was very close to the "measured" result that I am using in this paper. I no longer have access to the actual circuit board or the decades old measured

data.) So, the small, 0.22 pf stray capacitances of the pads where the series L and C components were soldered to the board apparently created the terrible filter response.

So, now what? We have to have those pads. Without them, the circuit could not be built.

Let's redesign the filter with those pad capacitances as fixed. We will adjust the values of everything else to work properly with the 0.22 pf stray capacitances of the board pads. This optimization results in the circuit shown in figure 6 and the results are in figure 7.

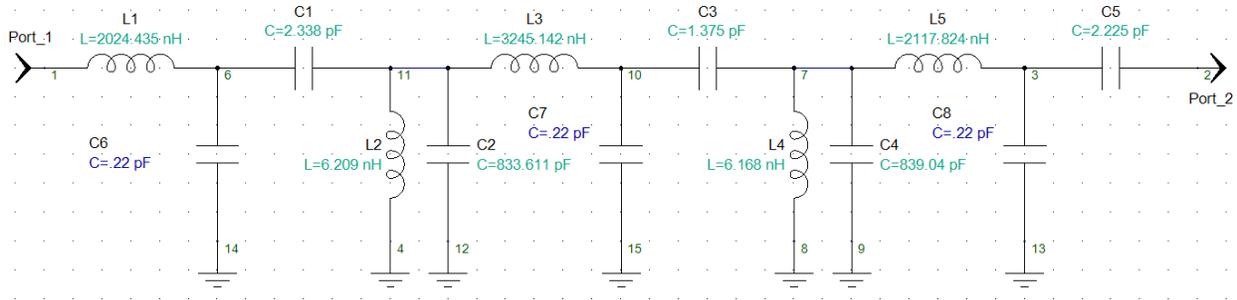


Figure 6 New circuit. The .22 pF capacitors are strays and not part of the populated parts

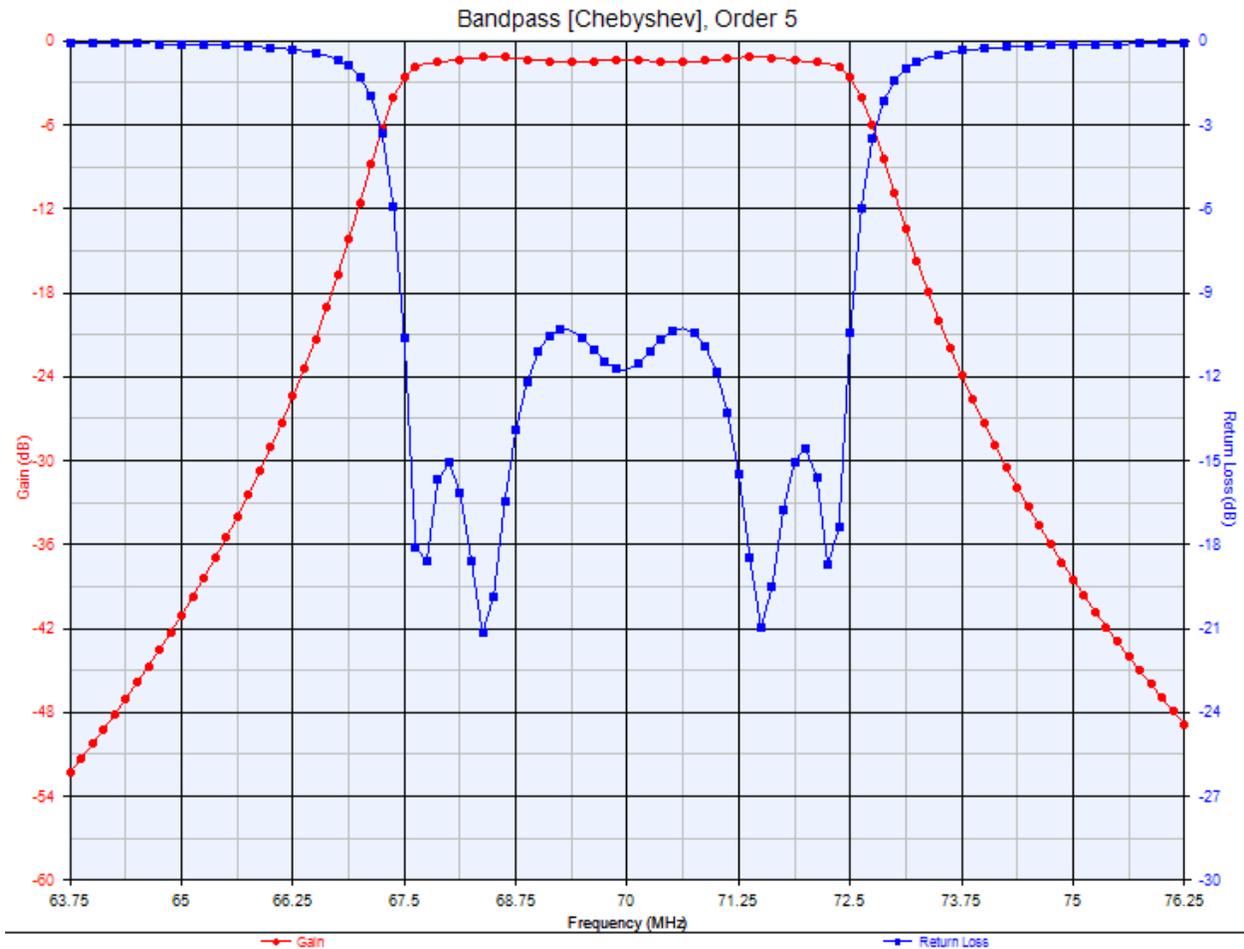


Figure 7 Simulated, optimized circuit response with .22 pF stray capacitances

While not identical to the original circuit simulation, this represents a usable filter which we built up and used. (Of course, any experienced engineer recognizes that the values in these simulations are ideal and not actual values of capacitance and inductance that can be purchased. But, by using standard value inductors and capacitors we were able to get adequate performance once we re-optimized the circuit given the .22 pF stray capacitances due to the physical pads on the boards that were necessary to connect the series L and C capacitors.)

Of course, we could have spent days changing values on an actual circuit board to eventually arrive at the necessary performance, but it was much faster (and thus less expensive) to use RF simulation software tools to do the troubleshooting and to come up with a great design.

To download an Adobe Acrobat copy of this paper, click [here](#).